

Lab 2: Pipelined CPU using verilog

Announcement

- Individual Lab
- Lab Deadline: 5/13 (Tue.) 23:59
- Demo:
 - Time slot: TBD
 - Show the execution of your program to TA and answer a few questions


Instructions

- Required Instruction Set
 - and, xor, sll, add, sub, mul, addi, srai
 - lw
 - sw
 - beq


Hardware Specification

- Register File: 32 Registers (**Write at the rising edge of the clock**), 32-bit
- Instruction Memory: 1KB
- Data Memory: 4 KBytes
- 5-stage pipeline (IF, ID, EX, MEM, WB)
- Hazard handling
 - Data hazard
 - Implement the **forwarding unit** to reduce or avoid the stall cycles
 - The data dependency instruction following **lw** must stall 1 cycle
 - No need to forward to ID stage
 - Control hazard
 - The instruction following **beq** instruction may need to stall 1 cycle
 - Pipeline **Flush**


Adding Pipeline Register

 

Forwarding Control

 

Handling Branch and Hazard

 

Control Signals

Instruction	ALUOp	operation	Funct7 field	Funct3 field	Desired ALU action	ALU control input
ld	00	load doubleword	XXXXXXXX	XXX	add	0010
sd	00	store doubleword	XXXXXXXX	XXX	add	0010
beq	01	branch if equal	XXXXXXXX	XXX	subtract	0110
R-type	10	add	0000000	000	add	0010
R-type	10	sub	0100000	000	subtract	0110
R-type	10	and	0000000	111	AND	0000
R-type	10	or	0000000	110	OR	0001

FIGURE 4.45 A copy of **Figure 4.12**. This figure shows how the ALU control bits are set depending on the ALUOp control bits and the different opcodes for the R-type instruction.

Control Signals

Instruction	Execution/address calculation stage control lines		Memory access stage control lines			Write-back stage control lines	
	ALUOp	ALUSrc	Branch	Mem-Read	Mem-Write	Reg-Write	Memto-Reg
R-format	10	0	0	0	0	1	0
ld	00	1	0	1	0	1	1
sd	00	1	0	0	1	0	X
beq	01	0	1	0	0	0	X

FIGURE 4.47 The values of the control lines are the same as in [Figure 4.18](#), but they have been shuffled into three groups corresponding to the last three pipeline stages.

Machine Code

funct7	rs2	rs1	funct3	rd	opcode	function
0000000	rs2	rs1	111	rd	0110011	and
0000000	rs2	rs1	100	rd	0110011	xor
0000000	rs2	rs1	001	rd	0110011	sll
0000000	rs2	rs1	000	rd	0110011	add
0100000	rs2	rs1	000	rd	0110011	sub
0000001	rs2	rs1	000	rd	0110011	mul
imm[11:0]		rs1	000	rd	0010011	addi
0100000	imm[4:0]	rs1	101	rd	0010011	srai
imm[11:0]		rs1	010	rd	0000011	lw
imm[11:5]	rs2	rs1	010	imm[4:0]	0100011	sw
imm[12,10:5]	rs2	rs1	000	imm[4:1,11]	1100011	beq

Be careful on your Imm_Gen !

Branch Address

`bne x10, x11, 2000` // if `x10 != x11`, go to location `2000ten = 0111 1101 0000`

0	111110	01011	01010	001	1000	0	1100111 1100011
imm[12]	imm[10:5]	rs2	rs1	funct3	imm[4:1]	imm[11]	opcode

(The opcode in textbook conflicts with RISC-V spec. Please follow this one)

next PC = current PC + Branch offset

Pipeline Register


 


FIGURE 4.33 The pipelined version of the datapath in Figure 4.31. The pipeline registers, in color, separate each pipeline stage. They are labeled by the stages that they separate; for example, the first is labeled *IF/ID* because it separates the instruction fetch and instruction decode stages. The registers must be wide enough to store all the data corresponding to the lines that go through them. For example, the *IF/ID* register must be 96 bits wide, because it must hold both the 32-bit instruction fetched from memory and the incremented 64-bit PC address. We will expand these registers over the course of this chapter, but for now the other three pipeline registers contain 256, 193, and 128 bits, respectively.

Adding Pipeline Register

 

Data Hazard and Forwarding

 


FIGURE 4.56 A pipelined sequence of instructions. Since the dependence between the load and the following instruction (and) goes backward in time, this hazard cannot be solved by forwarding. Hence, this combination must result in a stall by the hazard detection unit.

Data Hazard and Forwarding

 


FIGURE 4.56 A pipelined sequence of instructions. Since the dependence between the load and the following instruction (and) goes backward in time, this hazard cannot be solved by forwarding. Hence, this combination must result in a stall by the hazard detection unit.

Forwarding Unit

 


FIGURE 4.55 A close-up of the datapath in Figure 4.52 shows a 2:1 multiplexor, which has been added to select the signed immediate as an ALU input.

Forwarding Control

Mux control	Source	Explanation
ForwardA = 00	ID/EX	The first ALU operand comes from the register file.
ForwardA = 10	EX/MEM	The first ALU operand is forwarded from the prior ALU result.
ForwardA = 01	MEM/WB	The first ALU operand is forwarded from data memory or an earlier ALU result.
ForwardB = 00	ID/EX	The second ALU operand comes from the register file.
ForwardB = 10	EX/MEM	The second ALU operand is forwarded from the prior ALU result.
ForwardB = 01	MEM/WB	The second ALU operand is forwarded from data memory or an earlier ALU result.

FIGURE 4.53 The control values for the forwarding multiplexors in **Figure 4.52**. The signed immediate that is another input to the ALU is described in the *Elaboration* at the end of this section.

Forwarding Control

1. EX hazard:

```
if (EX/MEM.RegWrite  
and (EX/MEM.RegisterRd != 0)  
and (EX/MEM.RegisterRd == ID/EX.RegisterRs1)) ForwardA = 10
```


```
if (EX/MEM.RegWrite  
and (EX/MEM.RegisterRd != 0)  
and (EX/MEM.RegisterRd = ID/EX.RegisterRs2)) ForwardB = 10
```

2. MEM hazard:

```
if (MEM/WB.RegWrite  
and (MEM/WB.RegisterRd != 0)  
and not(EX/MEM.RegWrite and (EX/MEM.RegisterRd != 0)  
        and (EX/MEM.RegisterRd = ID/EX.RegisterRs1))  
and (MEM/WB.RegisterRd = ID/EX.RegisterRs1)) ForwardA = 01
```

```
if (MEM/WB.RegWrite  
and (MEM/WB.RegisterRd != 0)  
and not(EX/MEM.RegWrite and (EX/MEM.RegisterRd != 0)  
        and (EX/MEM.RegisterRd = ID/EX.RegisterRs2))  
and (MEM/WB.RegisterRd = ID/EX.RegisterRs2)) ForwardB = 01
```

Forwarding Control

 

Hazard Detection and Stall

 


FIGURE 4.57 The way stalls are really inserted into the pipeline. A bubble is inserted beginning in clock cycle 4, by changing the `and` instruction to a `nop`. Note that the `and` instruction is really fetched and decoded in clock cycles 2 and 3, but its EX stage is delayed until clock cycle 5 (versus the unstalled position in clock cycle 4). Likewise, the `or` instruction is fetched in clock cycle 3, but its ID stage is delayed until clock cycle 5 (versus the unstalled clock cycle 4 position). After insertion of the bubble, all the dependences go forward in time and no further hazards occur.

Stall & Flush

- Counted in testbench.v
- Can be changed depend on your own design


Example:

```
// put in your own signal to count stall and flush

if (CPU.HazardDetection.Stall_o == 1 && CPU.Control.Branch_o == 0)
    stall = stall + 1;

if (CPU.Flush == 1)
    flush = flush + 1;
```

Handling Branch and Hazard

 


testbench.v

- Initialize registers in all modules
- Load instruction.txt into instruction memory
- Create clock signal
- Dump Register files & Data memories in each cycle
- Count number of flush
- Do not modify any value initialization or message printing
- Print result to output.txt

Execution results

```
cycle =          0, Start = 1, Stall = 0, Flush = 0
PC =          0
Registers
x0 =          0, x8  =          0, x16 =          0, x24 =          -24
x1 =          0, x9  =          0, x17 =          0, x25 =          -25
x2 =          0, x10 =          0, x18 =          0, x26 =          -26
x3 =          0, x11 =          0, x19 =          0, x27 =          -27
x4 =          0, x12 =          0, x20 =          0, x28 =           56
x5 =          0, x13 =          0, x21 =          0, x29 =           58
x6 =          0, x14 =          0, x22 =          0, x30 =           60
x7 =          0, x15 =          0, x23 =          0, x31 =           62
Data Memory: 0x00 =           5
Data Memory: 0x04 =           6
Data Memory: 0x08 =          10
Data Memory: 0x0C =          18
Data Memory: 0x10 =          29
Data Memory: 0x14 =           0
Data Memory: 0x18 =           0
Data Memory: 0x1C =           0
```


Final Datapath

 

Grading Policy

- (80%) Programming
 - You will get 0 point if your code cannot be compiled
 - Grading at demo. You have to answer several questions about how you implement at demo. You may get 0 point on this part if you cannot clearly answer the questions (regarded as plagiarism)
- (20%) Report
 - Implementation of each modules
 - Difficulties encountered and solutions in this lab
 - Development environment
- Late policy: 10 points per day

Deadline

- 5/13 (Tue.) 23:59
- Late policy: 10 points per day

Submission Rule

- Submission format
 - <student_ID>_lab2/
 - <student_ID>_lab2/<student_ID>_lab2_report.pdf
 - <student_ID>_lab2/src/*.v
 - Pack the folder into a .zip file
 - e.g. b09902000_lab2.zip
 - Case sensitive (all alphabets being lower cases)

Directory Structure

We should see a single directory like following structure after we type

```
$ unzip bo9902000_lab2.zip
```

in Linux terminal:

```
bo9902000_lab2/
```

```
bo9902000_lab2/src
```

```
bo9902000_lab2/src/CPU.v
```

```
bo9902000_lab2/src/ALU.v
```

```
...
```

```
bo9902000_lab2/bo9902000_lab2_report.pdf
```